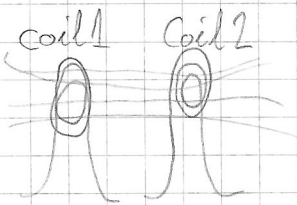


Inductance, Electromagnetic Oscillations and AC circuits

- A changing magnetic flux through a circuit induces EMF
- An electric current produces a magnetic field
 - Changing current in a circuit induce a current and EMF in another circuit
 - even an EMF in itself

Mutual inductance



If two coils of wire are placed in close proximity, a changing current in one will induce a current in the other

ϕ_{21} : Magnetic flux through each loop in coil 2 due to current in coil 1

$N_2\phi_{21}$: total magnetic flux in coil 2 due to coil 1

$$N_2\phi_{21} \propto I_1$$

$$M_{21} = \frac{N_2\phi_{21}}{I_1}$$

→ proportionality constant is called "mutual inductance"

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{21}}{dt} \quad (\text{Faraday's Law})$$

$$= -N_2 \frac{d}{dt} \left(\frac{M_{21} I_1}{N_2} \right) = -M_{21} \frac{dI_1}{dt}$$

$$\boxed{\mathcal{E}_2 = -M_{21} \frac{dI_1}{dt}}$$

Mutual inductance depends only on geometric factors such as size, shape, number of turns, relative positions


Conservation of energy $\rightarrow M_{21} = M_{12}$

$$\mathcal{E}_1 = -M \frac{dI_2}{dt}$$

$$\mathcal{E}_2 = -M \frac{dI_1}{dt}$$

The SI unit for mutual inductance is Henry (H), where $1\text{H} = 1\text{V}\cdot\text{s}/\text{A} = 1\Omega\cdot\text{s}$

Example Solenoid and Coil

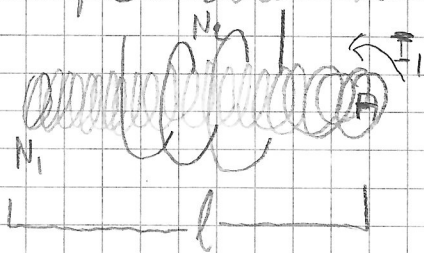

Along this solenoid of length l and cross sectional area A
Assume all the flux from coil 2 passes through coil 1


$$\Phi_{21} = BA = \mu_0 \frac{N_1}{l} I_1 A$$

$$M = \frac{N_2 \Phi_{21}}{I_1} = \frac{\mu_0 N_1 N_2 A}{l}$$

• M_{21} is easy to calculate, M_{12} is not since $M_{12} = M_{21}$ we use the simpler one

• If the second coil is inside the first A would refer to the area of second solenoid

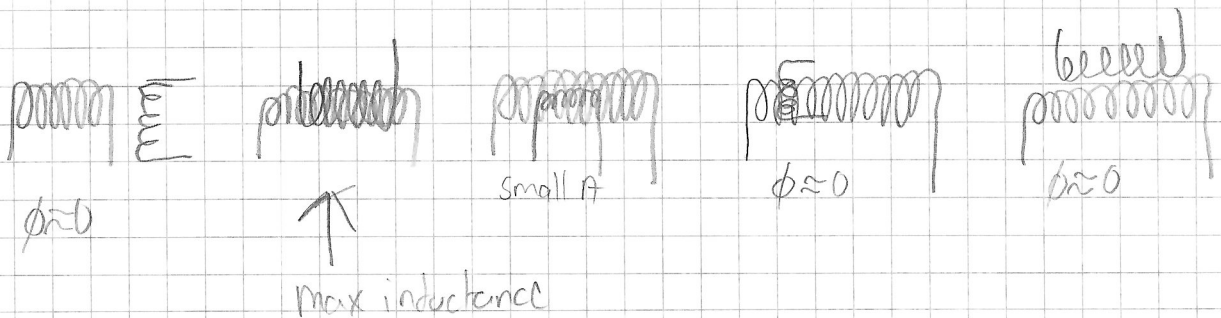- A transformer is a device which the coupling is maximised
- Mutual inductance is not always desirable, especially in electronic circuits which has fast switching, low current elements such as modern opcis



Self - Inductance

Lenz's law: When you try to change the current through the coil, an emf that opposes the change is induced

Increasing $I \rightarrow$ increasing magnetic flux
 \rightarrow opposing induced flux
 decreasing $I \rightarrow$ decreasing magnetic flux
 \rightarrow forbidding induced flux

The magnetic flux Φ_B passing through the N turns of coil is proportional to the current I passing the coil

→ we define self inductance L as

$$L = \frac{N\Phi_B}{I}$$

The induced emf in the coil is, from Faraday's law

$$\mathcal{E} = -N \frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$$


Like mutual inductance, self inductance is measured in Henry's

The magnitude of L depends on geometry and materials such as ferromagnetic core


Self inductance \equiv inductance

There is always some inductance in a circuit albeit small

Significant inductance → inductor

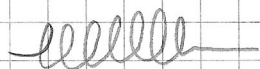

resistance of the inductor has to be handled separately

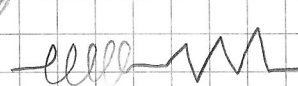 = realistic inductor

The inductance of resistors are minimized by non-inductive winding (winding back onto itself to cancel out ϕ)

$$\mathcal{E} = -L \frac{dI}{dt}$$

\rightarrow if ac current is fed this element will "resist" the current flow

Larger the L , larger the resistance (later we will also see that this also depends on the frequency of the ac current)

This is called reactance or impedance of the Inductor

a DC current through an Inductor will likely burn it out, since they usually have very small internal resistance

Common inductors: $1\mu\text{H} \rightarrow 1\text{H}$

Solenoid Inductance

- a) Determine a formula for the self inductance L of a tightly wrapped and long solenoid containing N turns of wire, in length l , with cross section area A

$$B = \frac{\mu_0 N I}{l} \quad (\text{ignoring the fringing})$$

$$\phi_B = BA = \frac{\mu_0 N I A}{l}$$


$$L = \frac{N \phi_B}{I} = \frac{\mu_0 N^2 A}{l}$$

b) $N=100, l=50\text{cm}, A=0.30\text{cm}^2$ (air filled)



$$L = \frac{(4\pi \times 10^{-7} \text{ T}\cdot\text{m/A})(100)^2 (3.0 \times 10^{-5} \text{ m}^2)}{(5.0 \times 10^{-2} \text{ m})} = 7.5 \mu\text{H}$$

(note: for an air filled solenoid, stray fields are significant \rightarrow this is just an approximation)

Direction of EMF in Inductors

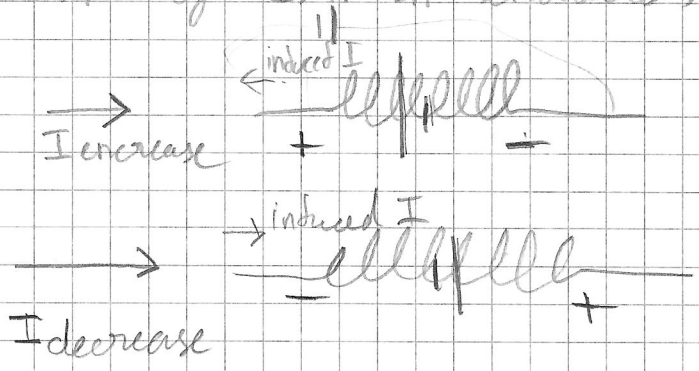

Coaxial cable inductance

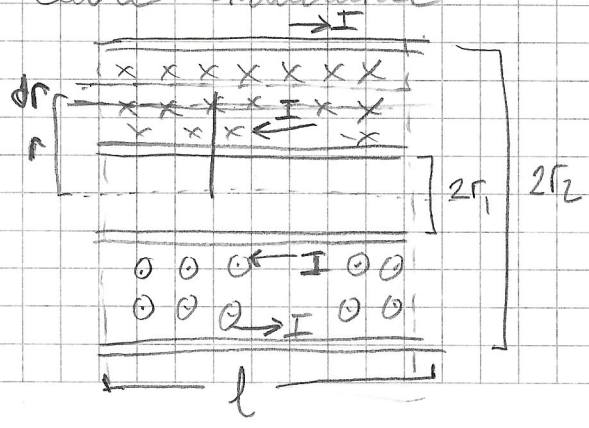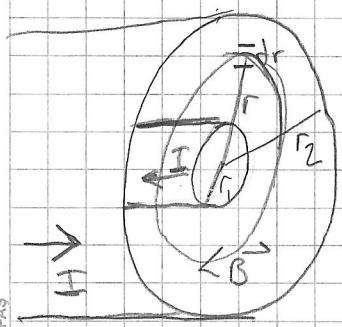

Determine the inductance per unit length of a coaxial cable. Assume the conductors are thin hollow tubes. Magnetic field inside both thin conductors can be ignored.

Ampère's law $\oint \vec{B} \cdot d\vec{\ell} = \mu_0 I$

\oint = circle at a distance r from the center

$$B = \frac{\mu_0 I}{2\pi r}$$

$$d\phi_B = B(l dr) = \frac{\mu_0 I l}{2\pi r} dr$$

$$\phi_B = \int d\phi_B = \frac{\mu_0 I l}{2\pi} \int_{r_1}^{r_2} \frac{dr}{r} = \frac{\mu_0 I l}{2\pi} \ln \frac{r_2}{r_1}$$

$$N = 1$$

$$L = \frac{\phi_B}{I} = \frac{\mu_0 l}{2\pi} \ln \frac{r_2}{r_1}$$

inductance per unit length is

$$\frac{L}{l} = \frac{\mu_0}{2\pi} \ln \frac{r_2}{r_1}$$

(note this does not depend on I)

Energy stored in a magnetic field

Energy stored in a magnetic field

L carrying I with $\frac{dI}{dt}$ rate of change

$$P = I\mathcal{E} = LI \frac{dI}{dt} \quad (\text{no - because we drive the solenoid externally})$$

$$dW = P dt = LI dI$$

$$W = \int dW = \int^I LI dI = \frac{1}{2} LI^2$$

(work-energy)

$$u = \frac{1}{2} LI^2 \quad (\text{similar to } u = \frac{1}{2} CV^2)$$

solenoid!

$$u = \frac{1}{2} LI^2 = \frac{1}{2} \left(\frac{\mu_0 N^2 A}{l} \right) \left(\frac{Bl}{\mu_0 N} \right)^2 = \frac{1}{2} \frac{B^2}{\mu_0} Al$$


(this energy can be thought to reside in the volume enclosed by the windings)

$$\text{energy density} = u = \frac{1}{2} \frac{B^2}{\mu_0}$$

This formula is valid in general!

$\mu_0 \rightarrow \mu$ for magnetic materials
(similar to $\frac{1}{2} \epsilon_0 E^2$)

LR circuits

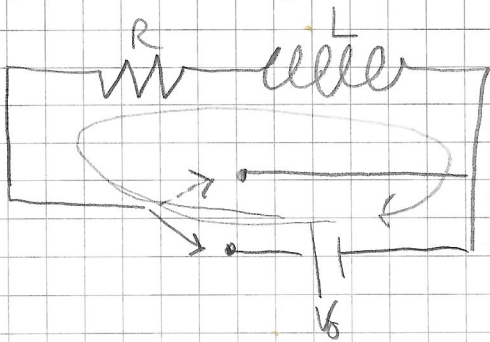

Kirchoff's at the instant switch is connected to battery

$$V_0 - IR - L \frac{dI}{dt} = 0$$

$$L \frac{dI}{dt} + RI = V_0$$

$$\int_{I=0}^I \frac{dI}{V_0 - IR} = \int_0^t \frac{dt}{L}$$

$$-\frac{1}{R} \ln \left(\frac{V_0 - IR}{V_0} \right) = \frac{t}{L}$$

$$I = \frac{V_0}{R} (1 - e^{-t/\tau})$$

$$\tau = \frac{L}{R} \quad (\text{time constant for LR circuit})$$

I reaches $(1 - 1/e) = 0.63$ after τ




When the switch is in discharge position

$$L \frac{dI}{dt} + RI = 0$$

$$\int_{I_0}^I \frac{dI}{I} = - \int_0^t \frac{R}{L} dt$$

$$\ln \frac{I}{I_0} = - \frac{R}{L} t$$

$$I = I_0 e^{-t/\tau}$$

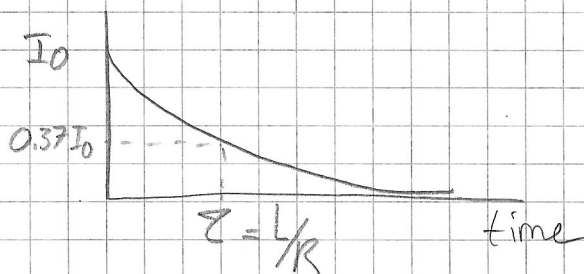


there is a reaction time when an electromagnet is turned on or off

LR circuit has similar behaviour to RC but the time constant is inversely proportional to R

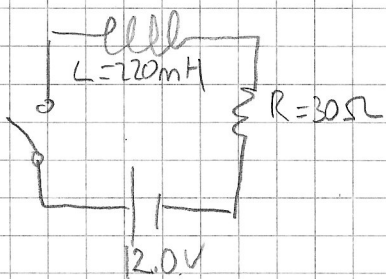Example

At $t=0$ a 12.0 V battery is connected in series with a 220 mH inductor and a total of 30 Ω resistance



a) current at $t=0$?

(inductor opposes the change)

so at $t=0$ $I=0$

b) what is the τ

$$\tau = L/R = 0.22\text{H}/30\Omega = 7.3\text{ms}$$

c) what is the max current

$$I_{\max} = V_0 / R = 12.0\text{V} / 30\Omega = 0.40\text{A}$$

d) How long will it take the current to reach half its maximum value

$$I = \frac{1}{2} I_{\max} = \frac{V_0}{2R}$$

$$1 - e^{-t/\tau} = \frac{1}{2}$$

$$e^{-t/\tau} = \frac{1}{2}$$

$$t = \tau \ln 2 = (7.3 \times 10^{-3}\text{s}) (0.69) = 5.0\text{ms}$$

e) At this instant, at what rate is energy being delivered by the battery?

$$I = I_{\max} / 2 = 200\text{mA}$$

$$P = IV = (0.20\text{A})(12\text{V}) = 2.4\text{W}$$

f) at what rate inductor stores energy?

$$U = \frac{1}{2} LI^2$$

$$\frac{dU}{dt} = LI \frac{dI}{dt} = I \left(L \frac{dI}{dt} \right) = I (V_0 - RI)$$

$$= 2.4\text{W} - (30\Omega)(0.20\text{A})^2 = 1.2\text{W}$$

lost to heat

